
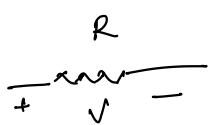


EE11G B Discussion


Circuit elements.

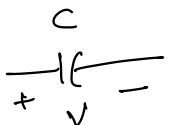

$$V = IR$$




$$i = C \frac{dV}{dt}$$

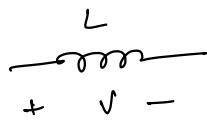


$$V = L \frac{di}{dt}$$


KCL, KVL →

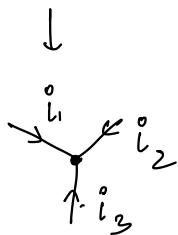

$$i_1 + i_2 + i_3 = 0$$

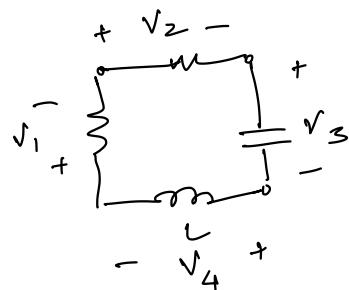


$$V_1 + V_2 + V_3 + V_4 = 0$$

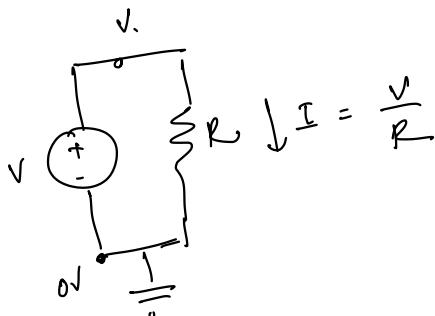

$$I = \frac{V}{R}$$


op-amps

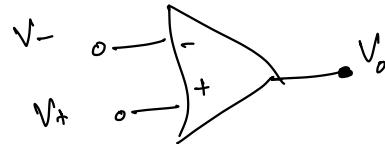


if $V_+ > V_- \rightarrow V_o$ is a large + value
 otherwise if $V_+ < V_- \rightarrow V_o$ is a large - value.

$$V_o = A(V_+ - V_-)$$

Negative feedback

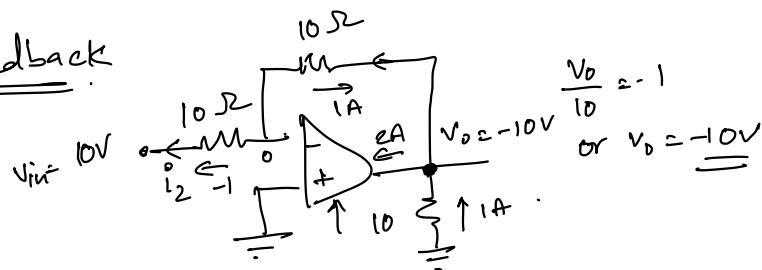

Golden Rules

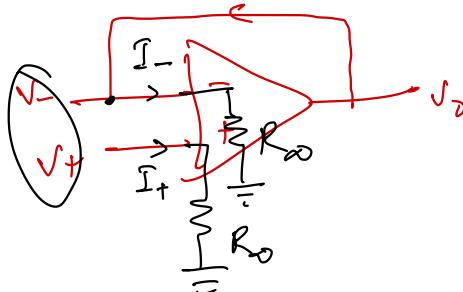

- $I_- = I_+ = 0$
- $V_- = V_+$

1 KCL

Consider the circuit shown below:


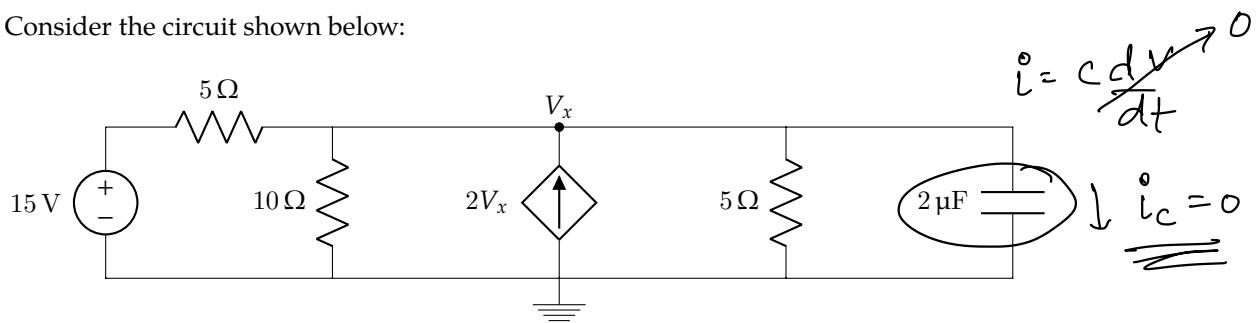


Figure 1: Adapted from Ulaby, Maharbiz, Furse. *Circuits*. Third Edition

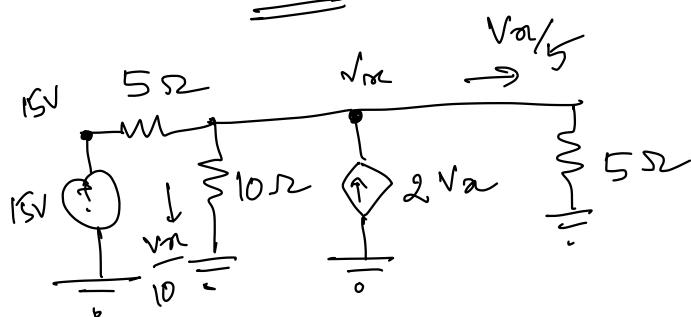Determine the voltage V_x at steady state.



$$-2V_a + \frac{V_a}{5} + \frac{V_a}{10} + \frac{V_a - 15}{5} = 0$$

$$-20V_a + 2V_a + V_a + 2V_a - 30 = 0$$

$$-15V_a - 30 = 0$$

$$\underline{\underline{V_a = -2V}}$$

2 KVL

Consider the circuit shown below:



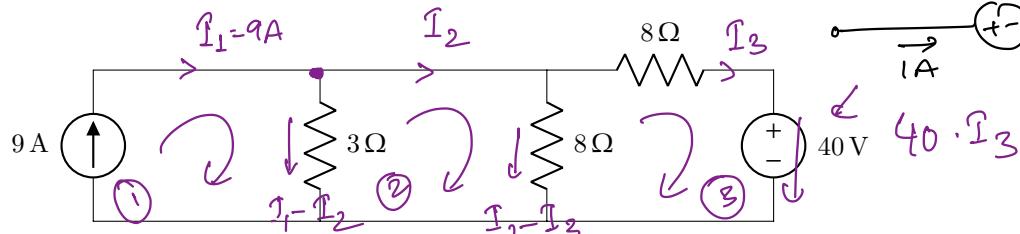
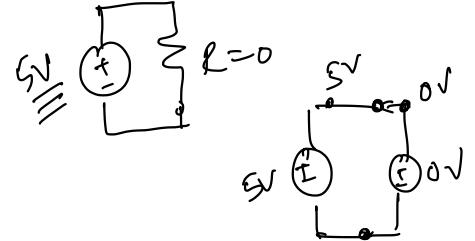
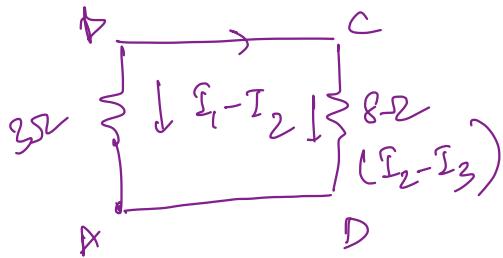


Figure 2: Adapted from Ulaby, Maharbiz, Furse. *Circuits*. Third Edition.

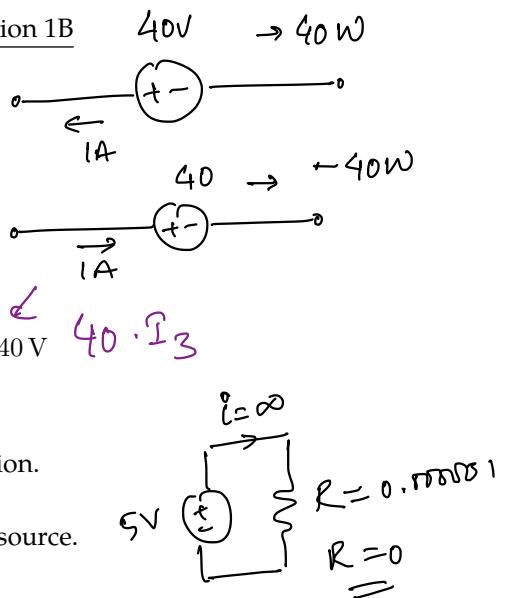Using KVL, determine the amount of power supplied by the voltage source.
Do not use superposition.


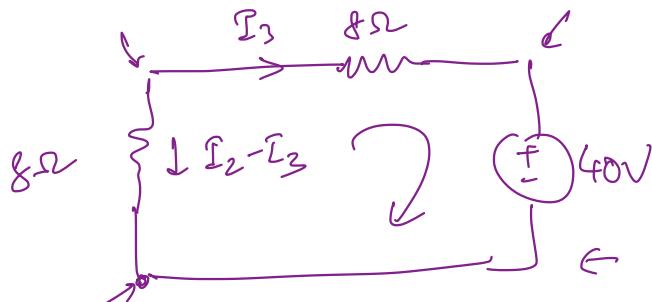
$$A \rightarrow B \quad 9(I_1 - I_2) - 8(I_2 - I_3) = 0 \quad ①$$




$$8(I_2 - I_3) - 8I_3 - 40 = 0 \quad ②$$

I₂

3 Op-Amp Review

Consider the circuit below

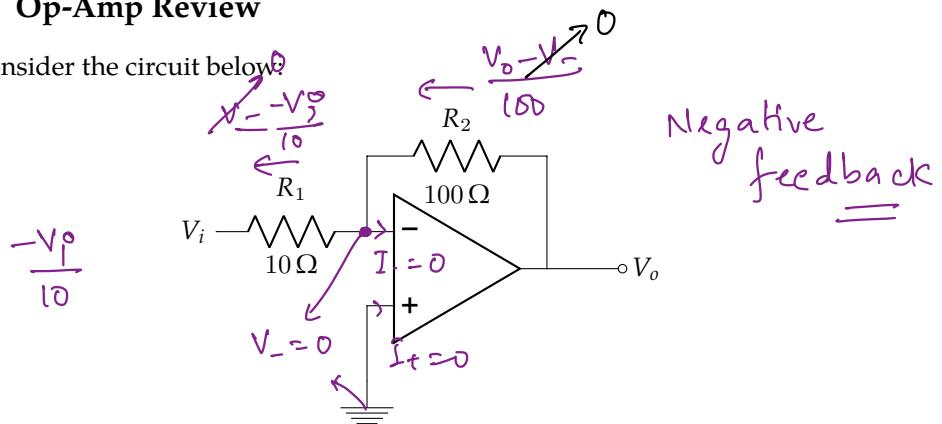


a) Calculate V_o if V_i if $V_i \neq 0.5 \text{ V}$.


$$\frac{V_o}{100} - \left(-\frac{V_i}{10} \right) = 0$$

$$\Rightarrow \frac{V_o}{100} = -\frac{V_i}{10} \quad \text{or} \quad \boxed{V_o = -10V_i}$$

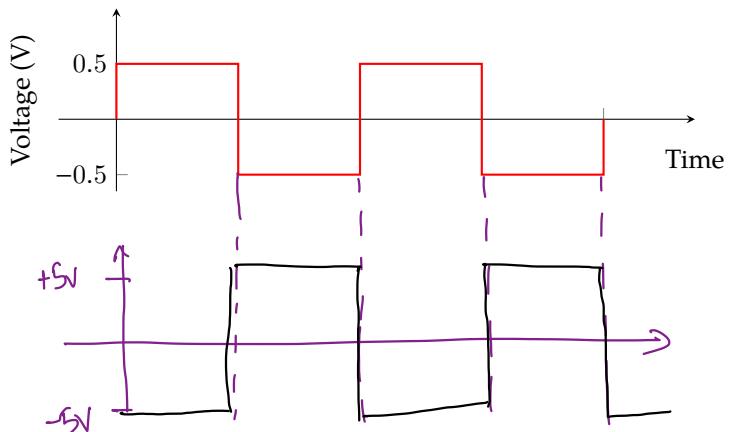
b) Sketch V_o if V_i is a square wave with $V_{pp} = 1 \text{ V}$.



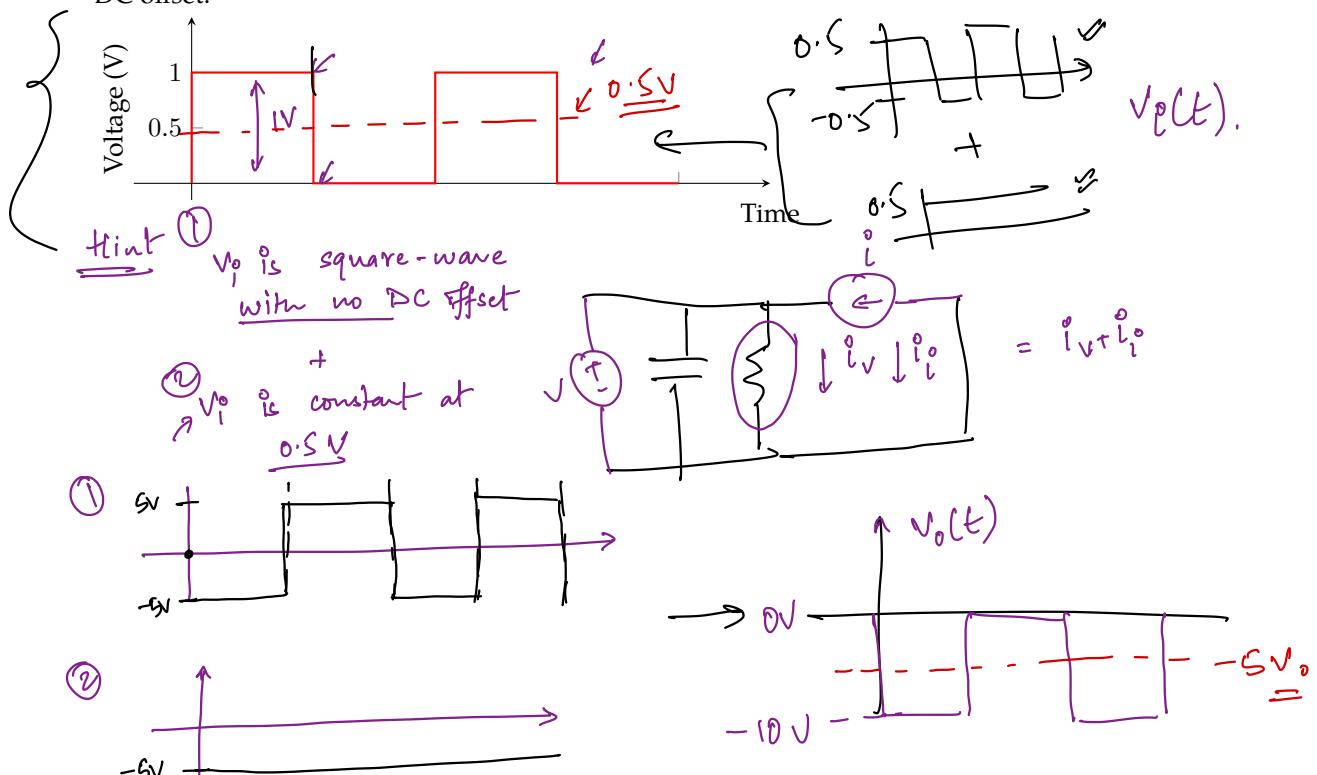- c) Use superposition to sketch V_o if V_i is a 1 V_{pp} square wave with a 0.5 V DC offset.



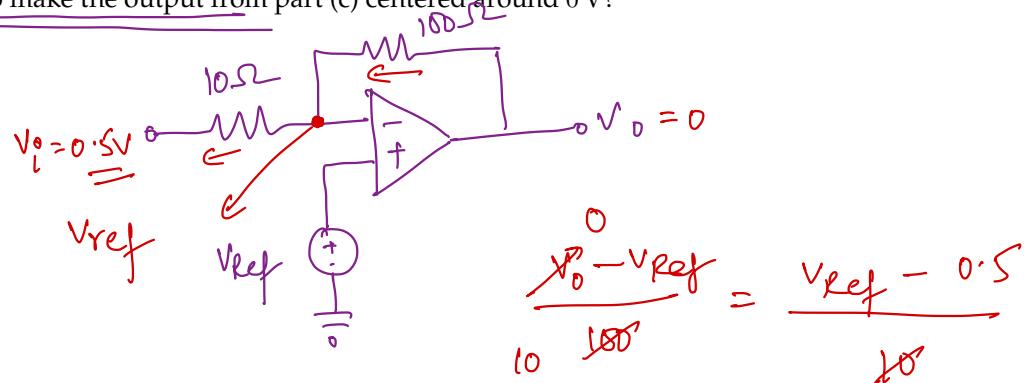- d) Consider the non-inverting input. What value could we replace ground with to make the output from part (c) centered around 0 V ?



$$-V_{ref} = 10V_{ref} - 5$$

$$V_{ref} = 5/11 \text{ V.}$$

- e) Suppose we only have a 1 V source, but still wish to center the output from (c) about 0 V. What circuit block should we place at the noninverting input to accomplish this goal?

